

Static Timing Analysis (STA)

Lecture #08: Flip-Flop Timing Parameters

Video Lecture [Link](#)

Static Timing Analysis (STA) – Flip-Flop Timing Parameters


The important timing parameters of a flip-flop are –

- 1) Clock-to-Q Delay*
- 2) Setup Time*
- 3) Hold Time*

VLSI Excellence

Static Timing Analysis (STA) – Flip-Flop Timing Parameters – Clock-to-Q Delay

 
- 1) **Clock-to-Q Delay** : The Active Clock “Edge” triggers the input to the output in a flip-flop and hence flop timing is calculated from the clock edge, and Clock-to-Q Delay is used for the flop timing.





Static Timing Analysis (STA) – Flip-Flop Timing Parameters – Setup Time

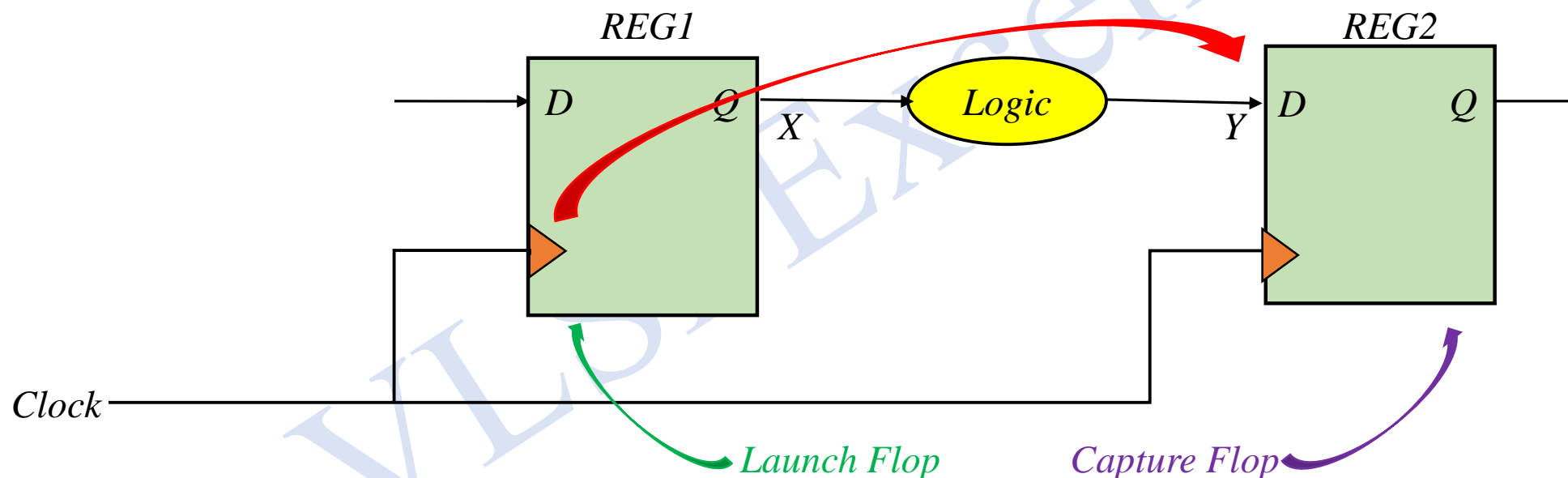2) Setup Time –


is the duration of time, the synchronous input data must be stable *before* the triggering edge of the clock (Either Positive OR Negative Edge Triggered Flip-Flop)



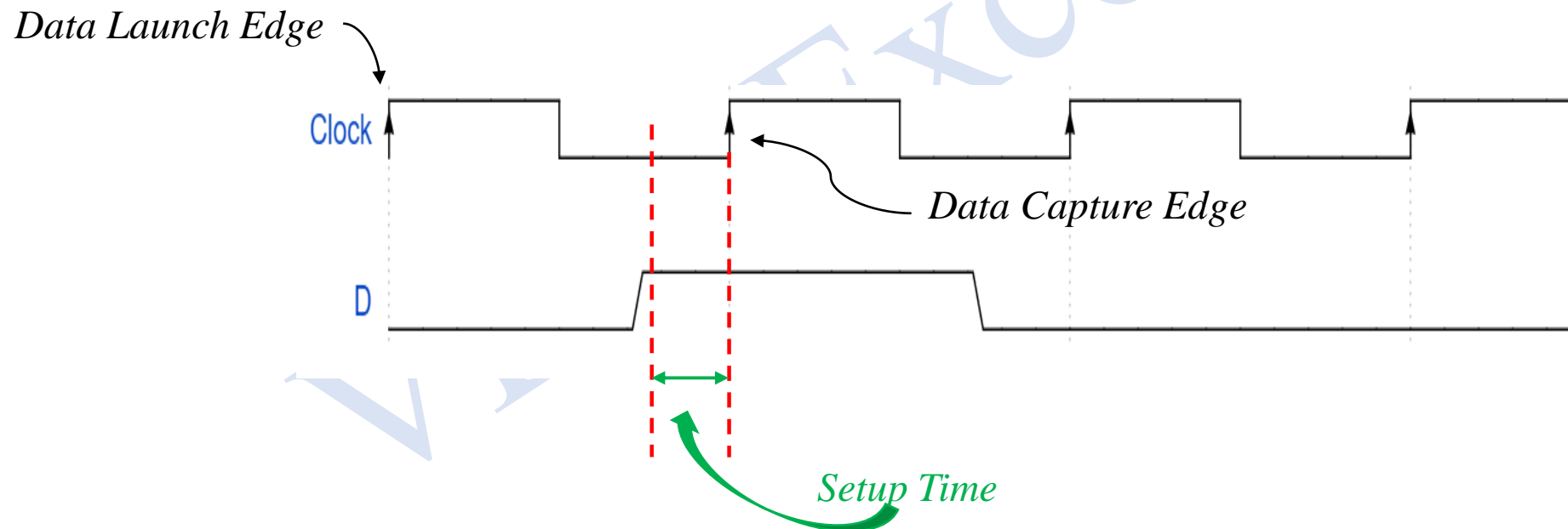 Static Timing Analysis (STA) – Flip-Flop Timing Parameters – Setup Time



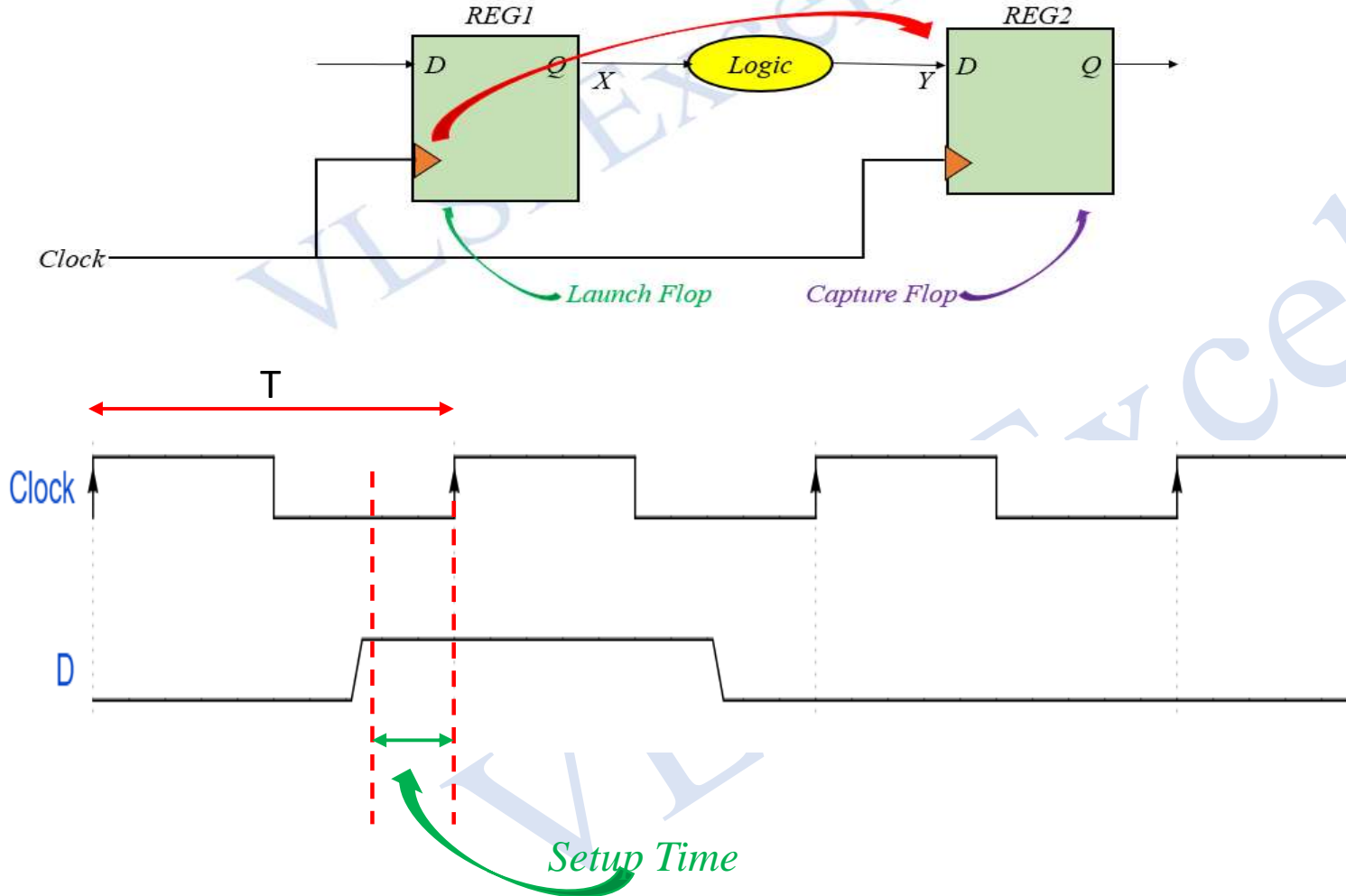Static Timing Analysis (STA) – Flip-Flop Timing Parameters – Setup Time




Note :

- 1) If Setup time is not met, data is not stored in the Flip-Flop
- 2) If **Data is Slow**, Setup Time will be violated, Data Lost !!
- 3) If Clock is **Speed UP**, Setup Time will be violated, Data Lost !!


Static Timing Analysis (STA) – Flip-Flop Timing Parameters – Setup Time

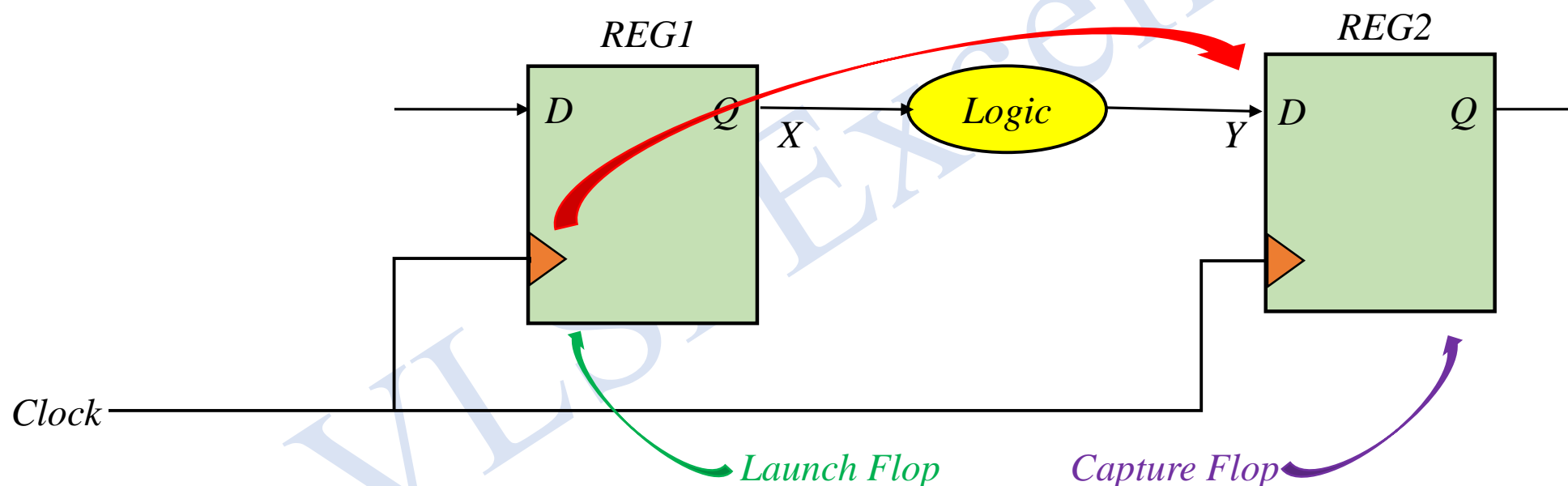3) Hold Time –


is the duration of time, the synchronous input data must be stable *after* the triggering edge of the clock (Either Positive OR Negative Edge Triggered Flip-Flop)



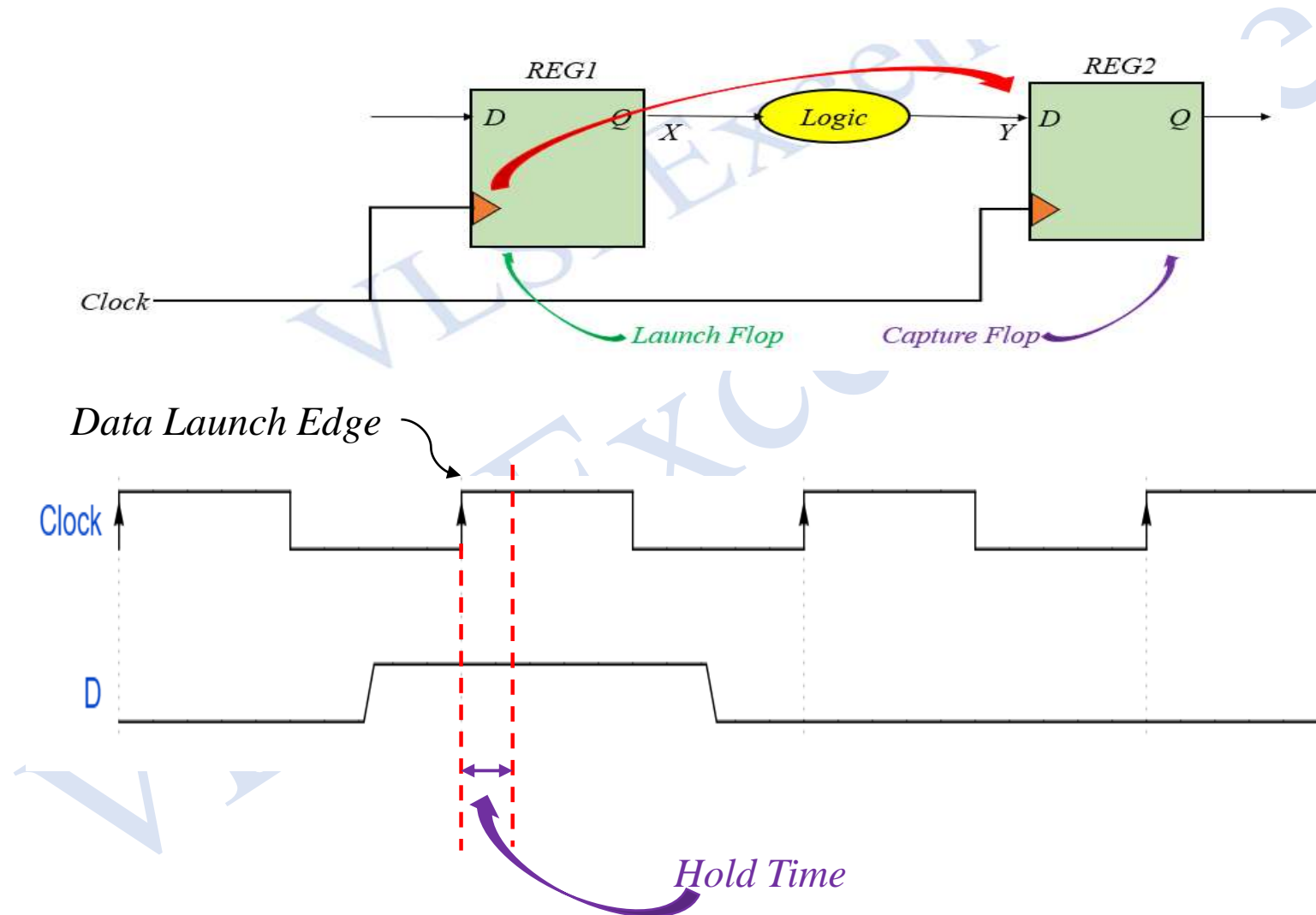Static Timing Analysis (STA) – Flip-Flop Timing Parameters – Hold Time



 Static Timing Analysis (STA) – Flip-Flop Timing Parameters – Hold Time



Note :

- 1) The Data Delay must be Greater than the Hold time of the Capture Flop for the Data to be safely stored in the Capture Flip-Flop
- 2) If the data starts changing immediately after the clock edge, Hold Time is Violated and Hence, Data Lost !!

Static Timing Analysis (STA) – Flip-Flop Timing Parameters – Setup and Hold in Timing Library

Example:

```
cell(DFF){
```

```
...
```

```
pin(D){
```

```
direction : input;
```

```
...
```

```
timing(){
```

```
related_pin : "CLK";
```

```
timing_type : setup_rising;
```

```
rise_constraint(setup_template_3x3){
```

```
index_1("0.012, 0.020, 0.125");
```

```
index_2("0.012, 0.020, 0.215");
```

```
values ("0.04562, 0.06753, 0.1234",/
```

```
"0.1234, 0.09876, 0.08967",/
```

```
"0.4321, 0.03456, 0.7865");}
```

```
}
```

```
...
```

```
timing(){
```

```
related_pin : "CLK";
```

```
timing_type : hold_rising;
```

```
rise_constraint(hold_template_3x3){
```

```
index_1("0.012, 0.020, 0.125");
```

```
index_2("0.012, 0.020, 0.215");
```

```
values ("-0.04562, -0.06753, -0.1234",/
```

```
"-0.1234, -0.09876, -0.08967",/
```

```
"-0.4321, -0.03456, -0.7865");}
```

```
}
```

```
}
```

```
}
```

Note:

index_1 = Data Transition

Index_2 = Clock Transition

Static Timing Analysis (STA) – Flip-Flop Timing Parameters – Setup and Hold in Timing Library

The setup and hold timing constraints for the synchronous pin of a sequential cell can be described in terms of two-dimensional table as shown in the previous slide.

The setup and hold timing constraints are on the input pin D with respect to the rising (active) edge of clock pin of the Flip-Flop.

The two-dimensional models are in terms of data and clock transition time at the **constrained_pin** (Data Pin D) and the **related_pin** (clock pin CK) respectively. Index 1 is showing data transition (D) at the rising edge and index 2 is showing the clock transition (CK) at the rising edge.

Example : With data D pin rise transition of 0.012ns and clock CK pin rise transition of 0.215ns so the setup constraint for the rising edge of the D pin is 0.1234ns (this value is read from the rise_constraint table).

Best Free VLSI Content

1. Verilog HDL Crash Course – [Link](#)
2. Static Timing Analysis (STA) – Theory Concepts – [Link](#)
3. Static Timing Analysis (STA) – Practice/Interview Questions – [Link](#)
4. Low Power VLSI Design – Theory Concepts – [Link](#)
5. Low Power VLSI Design (LPVLSI) – Practice/Interview Questions – [Link](#)
6. Digital ASIC Design Verilog Projects – [Link](#)

Please Like, Comment, Share & Subscribe [My Channel](#) in Order to Reach Out the Content to a Larger Audience.

Thanks !!