

Static Timing Analysis (STA)

Lecture #09: Flip-Flop Timing Constraints – Setup & Hold

Video Lecture [Link](#)


Static Timing Analysis (STA) – Flip-Flop Timing Constraints

There are two main problems which can arise in synchronous logic designs -

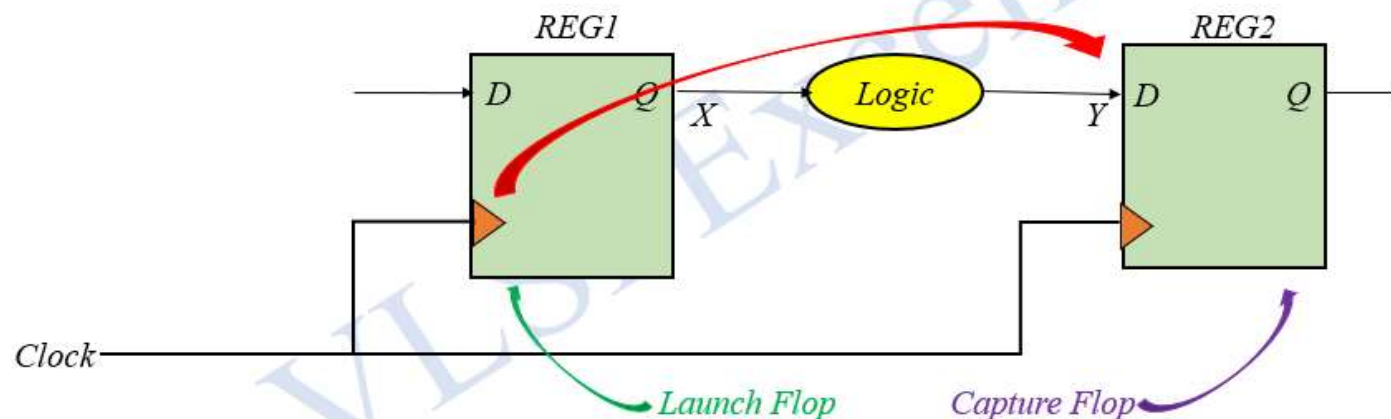1) Max Delay: The data does not have enough time to pass from one register to the next register before the next clock edge

- Max delay violations are the result of slow data path, including the register's T_{setup} time, therefore it is often called **Setup Path/Setup Constraint**


- A setup constraint specifies how much time is necessary for data to be available at the input of a sequential device before the clock edge that captures the data in the device.




Static Timing Analysis (STA) – Flip-Flop Timing Constraints

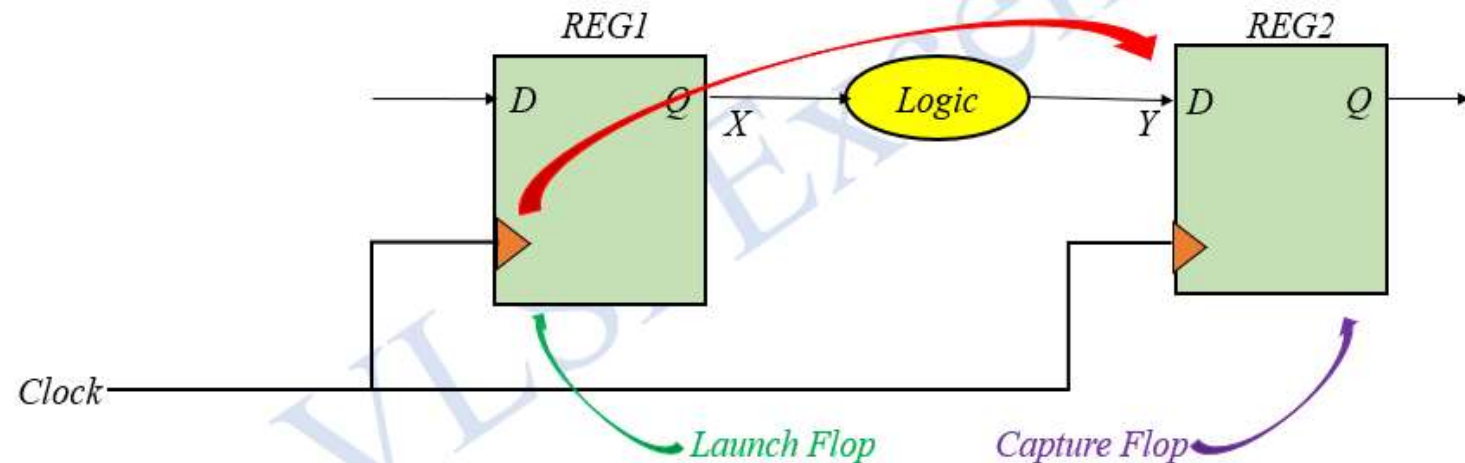2) **Min Delay**: The data path is so short that it passes through several registers during the same clock cycle


- Min delay violations are the result of short data path, causing the data to change before the register's T_{hold} time has passed, therefore it is often called the **Hold Path/Hold Constraint**
- A hold constraint specifies how much time is necessary for data to be stable at the input of a sequential device after the clock edge that captures the data in the device



 Static Timing Analysis (STA) – Flip-Flop Timing Constraints



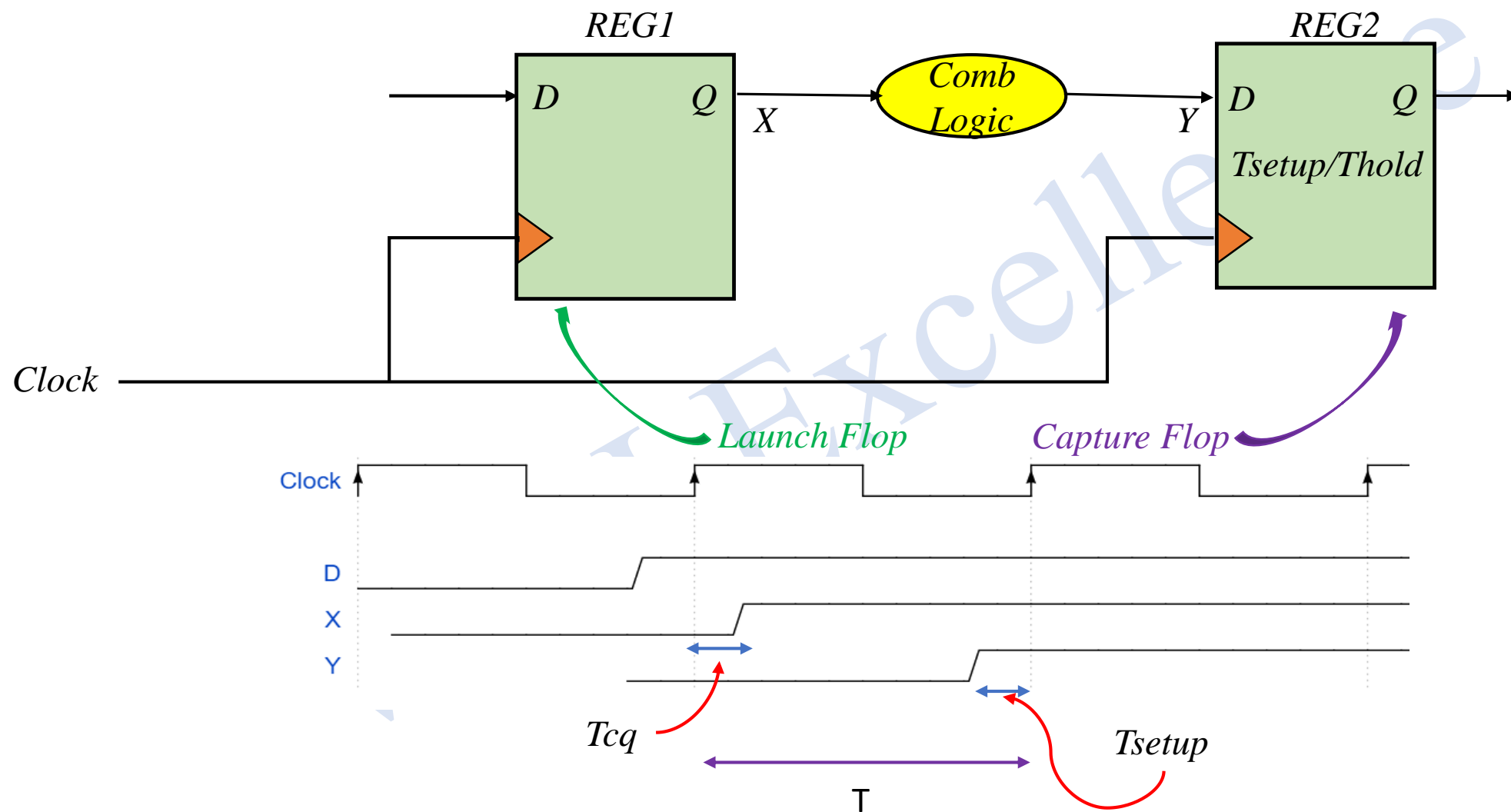Static Timing Analysis (STA) – Flip-Flop Timing Constraints – Max Delay/Setup



Static Timing Analysis (STA)-Flip-Flop Timing Constraints – Max Delay/Setup

1) After the clock rises, it takes T_{cq} for the data to propagate to point X.


2) Then the data goes through the delay of the logic to get to point Y

3) The data has to arrive at point Y, T_{setup} before the next clock edge


In general, our timing path is a race –

1) Between the data arrival, starting with the launching clock edge and

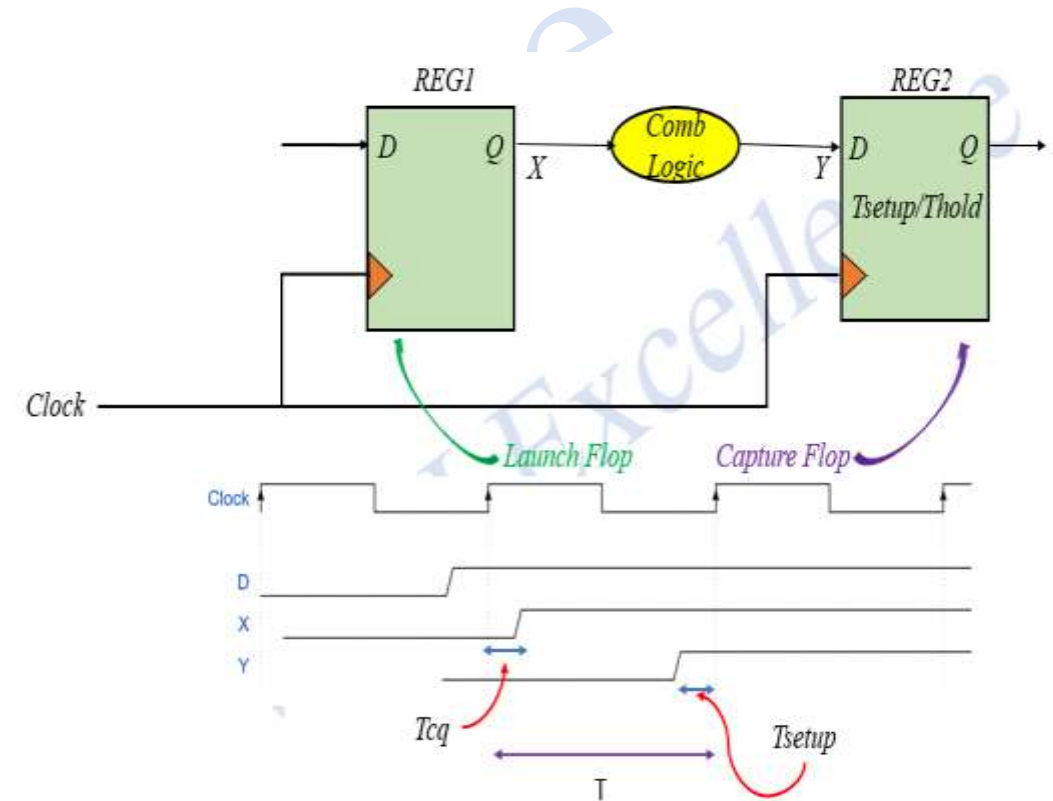2) The data capture, one clock period later



 Static Timing Analysis (STA) – Flip-Flop Timing Constraints – Min Delay/Hold



Static Timing Analysis (STA) – Flip-Flop Timing Constraints – Min Delay/Hold

1) Hold problems occur due to the logic changing before ***Thold*** has passed

2) This is not a function of a cycle time – it is relative to a single clock edge

In general,


1) The clock rises and the data at X changes after ***Tcq***

2) The data at Y changes after comb logic delay later

 3) Since the data at Y has to stay stable for ***Thold*** after the clock edge (for the second register).

The change at Y has to be at least ***Thold*** after the clock edge

- Hold time is the amount of time that REG1's old data must persist at the D input of REG2 after the clock edge



Best Free VLSI Content

1. Verilog HDL Crash Course – [Link](#)
2. Static Timing Analysis (STA) – Theory Concepts – [Link](#)
3. Static Timing Analysis (STA) – Practice/Interview Questions – [Link](#)
4. Low Power VLSI Design – Theory Concepts – [Link](#)
5. Low Power VLSI Design (LPVLSI) – Practice/Interview Questions – [Link](#)
6. Digital ASIC Design Verilog Projects – [Link](#)

Please Like, Comment, Share & Subscribe [My Channel](#) in Order to Reach Out the Content to a Larger Audience.

Thanks !!